


Project Report
CSC 3050 Simplified ALU

Wei Wu

118010335

April 10, 2020

The School of Science and Engineering

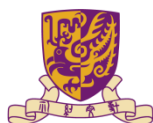

香港中文大學(深圳)
The Chinese University of Hong Kong, Shenzhen

1. Understandings of the Project

This project is about writing a simplified MIPS ALU using hardware description language Verilog. This project is divided into two modules. The first module is an instruction decoder. It decodes opcode (and funct for R-type instructions) of the MIPS instruction, and then generates aluctr and alusrc. The second module is an ALU. It takes aluctr, gr1, and operand2 (gr2 or sign-extended imm) as input. After corresponding calculation, it outputs the result and flags, including a zero flag, a negative flag, and an overflow flag.

2. The Implementations of the Project

2.1. The Big Picture Idea

At the very beginning, the hardware needs to generate control signals for the ALU from the input 32-bit MIPS instruction code. To be specific, the control signals include a 5-bit aluctr signal and a 1-bit alusrc signal. The aluctr signal determines the behavior of the ALU (add, sub, mult, ...), while the alusrc signal determines the second operand (gr2 or sign-extended imm). These signals can be generated according to the opcode (and funct for R-type instructions) of the instruction.

Then, according to the control signals, the ALU starts to handle the operation. Firstly, it calculates the result. After that, it sets the zero flag, the negative flag, and the overflow flag. In the end, it outputs both the result and the flags.

2.2. Implementation Details

2.2.0. Load and store

For most instructions, three registers are used: `reg_A`, `reg_B`, and `reg_C`.

The ALU loads the input `gr1` to `reg_A`. If `alusrc=0`, the ALU loads the input `gr2` to `reg_B`; else if `alusrc=1`, the ALU loads the sign-extended immediate to `reg_B`.

After calculation, the ALU stores the result in `reg_C`.

2.2.1. Special operations with other registers

For `mult` and `multu`, the register `hi` stores the higher 32 bits of the result, while the register `lo` stores the lower 32 bits of the result.

For `div` and `divu`, the register `hi` stores the remainder, while the register `lo` stores the quotient.

For `addiu`, `andi`, `ori`, `xori`, and `sltiu`, the register `imm0` stores the zero-extended immediate.

2.2.2. The control part

The control part (module `control_unit` in the code) takes both `opcode` and `funct` as input. It generates 2 control signals, namely `aluctr` and `alusrc`. The `aluctr` signal is 5-bit long. It determines the behavior of the ALU (`add`, `sub`, `mult`, ...).

While the `alusrc` signal is 1-bit long. It determines the source of the second operand (`gr2` or sign-extended `imm`).

If `opcode` is 0 (R-type instructions and `BEQ`, `BNE`), the `alusrc` signal will be set to 0, which indicates that the second operand (`reg_B`) should be `gr2`. Else, if the `opcode` is not 0 (other I-type or J-type instructions), the `alusrc` signal will be set

to 1, which indicates that the second operand (reg_B) should be the sign-extended immediate.

Furthermore, the required instructions are sorted by their ALU behaviors. Each distinct ALU behavior is mapped to an aluctr code. For example, both sub and beq correspond to ALU subtraction. Thus, they should share the same aluctr code.

In this project, we just made up all the aluctr codes. The correspondence between aluctr and ALU behaviors are illustrated in the following table.

0: add / addi / lw / sw	1: addu / addiu	2: sub / beq / bne	3: subu
4: mult	5: multu	6: div	7: divu
8: and	9: nor	10: or	11: xor
12: slt / slti	13: sltu / sltiu	14: sll	15: sllv
16: srl	17: srlv	18: sra	19: srav
20: andi	21: ori	22: xori	

2.2.3. Sign-extension and zero-extension

According to the MIPS ISA, the immediate is sign-extended and then transferred to the ALU. The sign-extended immediate can be used directly when the instruction is addi, beq, bne, ... However, when it comes to instructions like andi, ori, xori, ..., the zero-extended immediate is needed. Therefore, inside the ALU, we need to generate the zero-extended immediate from the input sign-extended immediate. Also, an additional register imm0 is needed to store the

zero-extended immediate.

For zero-extension, we only need to concatenate 16 0's with the immediate. The

Verilog code is like:

```
{{16{1'b0}}, reg_B[15:0]}
```

For sign-extension, we need to extend the immediate with its sign bit (MSB).

The Verilog code is like:

```
{{16{imm[15]}}, imm}
```

2.2.4. The negative flag

For signed operations, the negative flag indicates whether the result is negative.

It simply equals the sign bit (MSB) of the result. For unsigned operations, the negative flag is not important. We just set it to be 0.

2.2.5. The zero flag

The zero flag indicates whether the result is equal to zero. It is a signal for branch instructions.

2.2.6. The overflow flag

For instructions like add, sub, addi, ..., the overflow flag indicates whether an overflow exception happens. For other instructions, it is not important. We just set it to be 0.


In the MIPS ALU, the 32-bit full adder consists of 32 1-bit full adders. To detect overflow, we can simply compare the 30th carry-out and the 31st carry-out (In other words, carry into MSB and carry out of MSB). If the 30th carry-out is not equal to the 31st carry-out, an overflow occurs.

In my program, I did not use a 32-bit full adder. Instead, I just use “reg_A + reg_B”. Therefore, I used an additional 1-bit register called bit32 to detect overflow. The code is

```
{bit32, reg_C} = {reg_A[31], reg_A} + {reg_B[31], reg_B};  
overflow = bit32 ^ reg_C[31];
```

The mechanism is very similar. First, concatenate reg_A and reg_B to their MSB, respectively. Then, add them up. Store the result in the reg_C concatenated to the extra 1-bit register bit32. If bit32 is not equal to reg_C[31], an overflow occurs.

2.3. Block Diagram

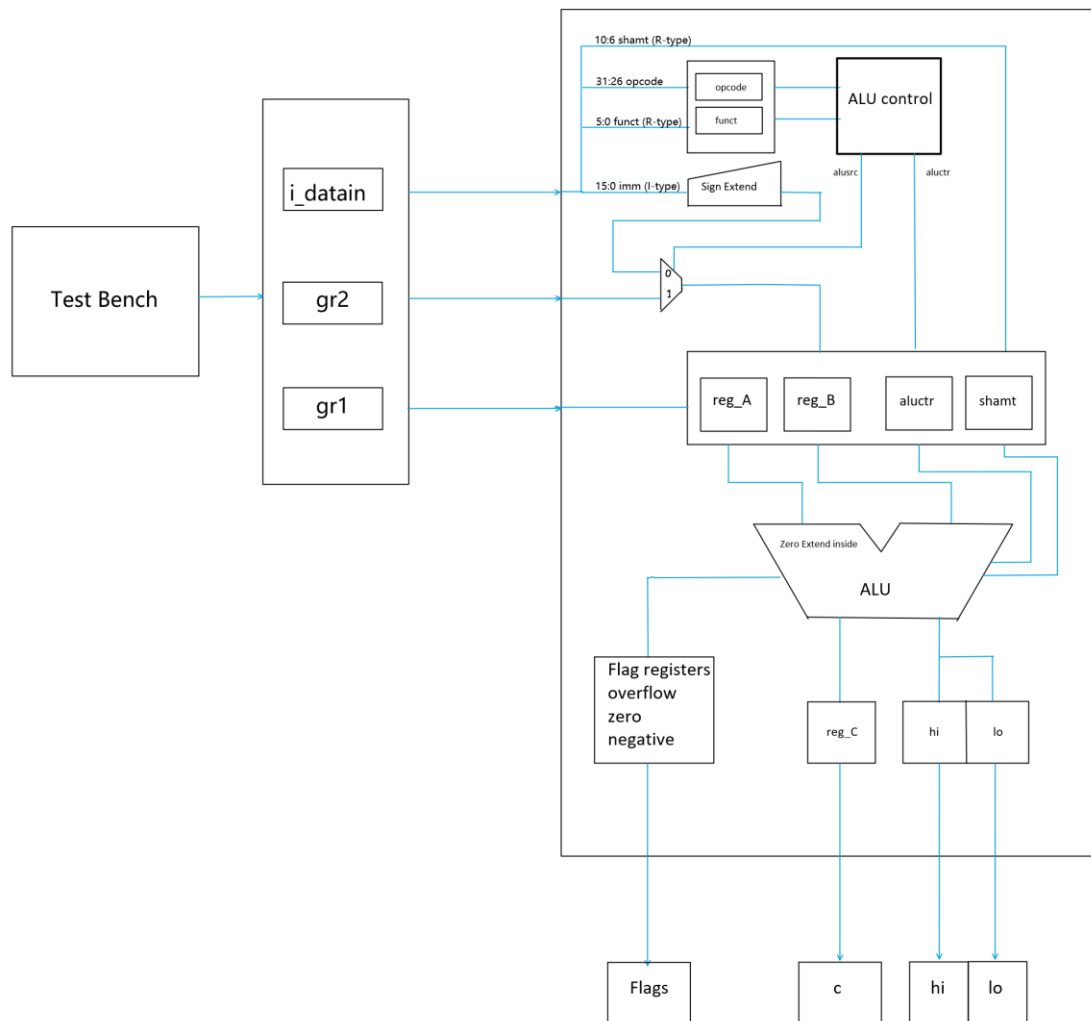

Registers:

In main module:

```
//Instruction Decoding
reg [5:0] opcode, funct;

//shamt
reg unsigned [4:0] shamt;

//Sign-extended immediate
reg [31:0] imm;

//When alusrc = 0, operand2 = gr2
//When alusrc = 1, operand2 = imm
reg [31:0] operand2;
```

In ALU Control module:

```
//Registers for operand1, operand2, and result
reg signed [31:0] reg_A, reg_B, reg_C;

//Registers for the flags
reg zero, negative, overflow;

//Register hi and lo.
//They are used for MULT, MULTU, DIV, DIVU
reg [31:0] hi, lo;

//Unsigned registers for MULTU, DIVU, SLTU, SLTIU
reg [31:0] reg_B_u, reg_A_u;

//Zero-extended imm
reg [31:0] imm0;

//Register which is used to detect overflow
reg bit32;
```

In the control_unit module

```
/*
alucr is made up
It starts from 0b0_0000
*/
reg [5:0] alucr;

//alusrc = 0 : from register
//alusrc = 1 : from extended immediate
reg alusrc;
```


2.4. Explanation of Instructions


2.4.0. Testing Environment

Windows 10 x64

iVerilog v11-20190809 x64

2.4.1. ADD / ADDI

Hardware: 32-bit full adder

 

Theory: The 32-bit full adder is composed of 32 1-bit full adders. The inputs $a[31:0]$ and $b[31:0]$ are `reg_A` and `reg_B`. For addition, `cin` is 0.

Registers: `reg_A`, `reg_B`, `reg_C`

Result: $c = gr1 + gr2$ / $c = gr1 + [\text{sign-extended}] \text{ imm}$

Overflow flag: Set if an overflow occurs.

Zero flag: Set if `reg_C = 0`.

Negative flag: `reg_C[31]`

Test Result:

```
//ADD: 1 + 8 = 9
#10 i_datain<=32'b000000_00011_00010_00001_00000_100000;
gr1<=32'b0000_0000_0000_0000_0000_0000_0000_0001;
```

```
gr2<=32'b0000_0000_0000_0000_0000_0000_0000_1000;

//ADD: 2 + -2 = 0 zero
#10 i_datain<=32'b000000_00011_00010_00001_00000_100000;
gr1<=32'b0000_0000_0000_0000_0000_0000_0000_0010;
gr2<=32'b1111_1111_1111_1111_1111_1111_1111_1110;

//ADD: -2 + -1 = -3 negative
#10 i_datain<=32'b000000_00011_00010_00001_00000_100000;
gr1<=32'b1111_1111_1111_1111_1111_1111_1111_1110;
gr2<=32'b1111_1111_1111_1111_1111_1111_1111_1111;

//ADD: -1 + -2147483648 = overflow
#10 i_datain<=32'b000000_00011_00010_00001_00000_100000;
gr1<=32'b1111_1111_1111_1111_1111_1111_1111_1111;
gr2<=32'b1000_0000_0000_0000_0000_0000_0000_0000;

//ADD: 2147483647 + 8 = overflow
#10 i_datain<=32'b000000_00011_00010_00001_00000_100000;
gr1<=32'b0111_1111_1111_1111_1111_1111_1111_1111;
gr2<=32'b0000_0000_0000_0000_0000_0000_0000_1000;
```

[illegible]

```
//ADDI: 7 + 8 = 15
#10 i_datain<=32'b001000_00011_00010_0000000000001000;
gr1<=32'b0000_0000_0000_0000_0000_0000_0000_0111;
gr2<=32'b0000_0000_0000_0000_0000_0000_0000_0000;

//ADDI: 3 + -3 = 0 zero
#10 i_datain<=32'b001000_00011_00010_1111111111111101;
gr1<=32'b0000_0000_0000_0000_0000_0000_0000_0011;
gr2<=32'b0000_0000_0000_0000_0000_0000_0000_0000;

//ADDI: 1 + -64 = -63 negative
#10 i_datain<=32'b001000_00011_00010_1111111111100000;
gr1<=32'b0000_0000_0000_0000_0000_0000_0000_0001;
gr2<=32'b0000_0000_0000_0000_0000_0000_0000_0000;

//ADDI: -2147483648 + -1 = overflow
#10 i_datain<=32'b001000_00011_00010_1111111111111111;
gr1<=32'b1000_0000_0000_0000_0000_0000_0000_0000;
gr2<=32'b0000_0000_0000_0000_0000_0000_0000_0000;
```

[illegible]

2.4.2. ADDU / ADDIU

Hardware: 32-bit full adder

Registers: reg_A, reg_B, reg_C / c = gr1 + [sign-extended] imm

Result: $c = gr1 + gr2$

Overflow flag: 0

Zero flag: Set if reg_C = 0.

Negative flag: 0

Test Result:

```
//ADDU: 2147483647 + 8 = 2147483655
#10 i_datain<=32'b0000000_00011_00010_00001_00000_100001;
gr1<=32'b0111_1111_1111_1111_1111_1111_1111_1111;
gr2<=32'b0000_0000_0000_0000_0000_0000_0000_1000;

//ADDIU: 2147483647 + 8 = 2147483655
#10 i_datain<=32'b001001_00011_00010_00000000000001000;
gr1<=32'b0111_1111_1111_1111_1111_1111_1111_1111;
gr2<=32'b0000_0000_0000_0000_0000_0000_0000_0000;
```

[illegible]

2.4.3. SUB

Hardware: 32-bit full adder, invertor

Theory: Subtraction can be done by adding the 2's complement of the subtrahend. First, use the 32-bit inverter to get the 1's complement of reg B.

Then, the inputs $a[31:0]$ and $b[31:0]$ are reg A and 1's complement of reg B.

For subtraction, cin is 1. This is because adding 1 to the 1's complement gives the 2's complement.

Registers: reg A, reg B, reg C

3. Shift {hi, lo} right by 1 bit

For negative numbers:

1. Remember the sign of each operand.
2. Convert any negative number to its 2's complement (absolute value).
3. Do the multiplication as the positive numbers.
4. If one operand is negative and the other is positive, convert the result to its 2's complement.

Registers: reg_A, reg_B, hi, lo

Result: {hi, lo} = gr1 * gr2

Overflow flag: 0

Zero flag: Set if {hi, lo} = 0.

Negative flag: hi[31]

Test Result:

```
//MULT: 2 * 4 = 8
#10 i_datain<=32'b000000_00011_00010_00001_00000_011000;
gr1<=32'b0000_0000_0000_0000_0000_0000_0010;
gr2<=32'b0000_0000_0000_0000_0000_0000_0100;

//MULT: 2 * 0 = 0 zero
#10 i_datain<=32'b000000_00011_00010_00001_00000_011000;
gr1<=32'b0000_0000_0000_0000_0000_0000_0010;
gr2<=32'b0000_0000_0000_0000_0000_0000_0000;

//MULT: -2 * 4 = -8 negative
#10 i_datain<=32'b000000_00011_00010_00001_00000_011000;
gr1<=32'b1111_1111_1111_1111_1111_1111_1110;
gr2<=32'b0000_0000_0000_0000_0000_0000_0100;

//MULT: 16777215 * 16777215 = 281474943156225
#10 i_datain<=32'b000000_00011_00010_00001_00000_011000;
gr1<=32'b0000_0000_1111_1111_1111_1111_1111;
```

```
gr2<=32'b0000_0000_1111_1111_1111_1111_1111_1111;
```

Instruction: op: func: ALUctr: ALUSrc:		gr1	:	gr2	:	imm	:	shamt:	:	e	:	hi	:	lo	:	zero	:	negative	:	overflow
XXXXXXXXXX	XX	XX	:	XXXXXXXXXXXXXXXXXXXXXXXXXXXXXXXXXXXX	:	XXXXXXXXXXXXXXXXXXXXXXXXXXXXXXXXXXXX	:	XXXXXXXXXXXXXXXXXXXX	:	XXXXXXXXXXXXXXXXXXXXXXXXXXXXXXXXXXXX	:	XXXXXXXXXXXXXXXXXXXX	:	XXXXXXXXXXXXXXXXXXXX	:		:		:	
00e20818:00	18	04	:	0:000000000000000000000000000000000101	:	0:000000000000000000000000000000000100	:	0000100000011000	:	000000	:	XXXXXXXXXXXXXXXXXXXXXXXXXXXXXXXXXXXX	:	0000000000:0000000000	:	0	:	0	:	0
00e20818:00	18	04	:	0:000000000000000000000000000000000101	:	0:000000000000000000000000000000000000	:	0000000000011000	:	000000	:	XXXXXXXXXXXXXXXXXXXXXXXXXXXXXXXXXXXX	:	0000000000:0000000000	:	1	:	0	:	0
00e20818:00	18	04	:	0:111111111111111111111111111111111111	:	0:000000000000000000000000000000000101	:	0000000000011000	:	000000	:	XXXXXXXXXXXXXXXXXXXXXXXXXXXXXXXXXXXX	:	ffffffffff:ffffffffff	:	0	:	1	:	0
00e20818:00	18	04	:	0:111111111111111111111111111111111111	:	0:0000000001111111111111111111111111111111	:	0000000000011000	:	000000	:	XXXXXXXXXXXXXXXXXXXXXXXXXXXXXXXXXXXX	:	0000ffff:fe000001	:	0	:	0	:	0

2.4.6. MULTU

Hardware: 32-bit x 32-bit multiplier

Theory: Since the operands are unsigned, use unsigned registers for them.

Registers: reg_A_u, reg_B_u, hi, lo

Result: $\{hi, lo\} = gr1 * gr2$

Overflow flag: 0

Zero flag: Set if $\{\text{hi}, \text{lo}\} = 0$.

Negative flag: 0


Test Result:

```
//MULTU: 2147483649 * 1 = 2147483649
#10 i_datain<=32'b0000000_00011_00010_00001_00000_011001;
gr1<=32'b1000_0000_0000_0000_0000_0000_0000_0001;
gr2<=32'b0000_0000_0000_0000_0000_0000_0000_0001;
```

[illegible]

2.4.7. DIV

Hardware: 32-bit / 32-bit divisor

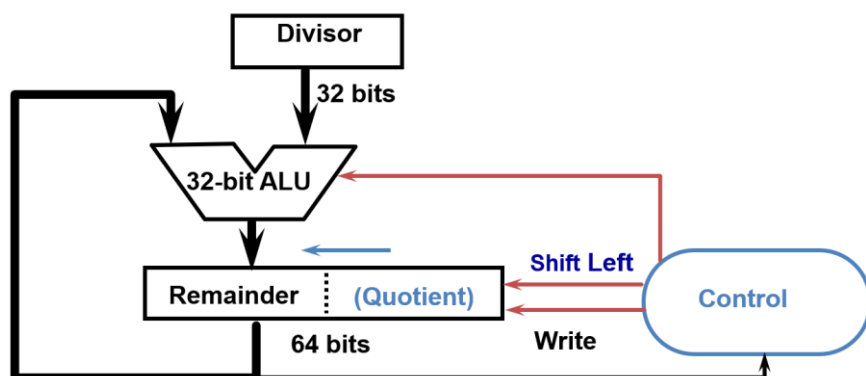

Theory:

Since a 32-bit / 32-bit division gets a 32-bit quotient and a 32-bit remainder, we need two 32-bit registers hi and lo to store the result.

Algorithm

For positive numbers:

1. Place the dividend (reg_A) into register lo. Set register hi to be 0. Shift register {hi, lo} left by 1 bit.

Repeat the following steps for 32 times:

2. Subtract divisor (reg_B) from the register hi. Place the result in register hi.
3. If register hi ≥ 0 , shift register {hi, lo} left by 1 bit. Set lo[0] to be 1.
Else if register hi < 0 , restore original value by adding Divisor divisor (reg_B) to register hi. Place sum in register hi. Also shift register {hi, lo} left by 1 bit. Set lo[0] to be 0.
4. Shift register hi right by 1 bit.

For negative numbers, do the following steps:

1. Remember the sign of each operand.
2. Convert any negative number to its 2's complement (absolute value).
3. Do the division as the positive numbers.
4. If one operand is negative and the other is positive, convert the result to its 2's complement.

[illegible]

2.4.10. NOR

Hardware: NOR gates

Theory: NOR can be done by bitwise operation.

Registers: reg_A, reg_B, reg_C

Result: $c = \sim (\text{gr1} \mid \text{gr2})$

Overflow flag: 0

Zero flag: Set if reg_C = 0.

Negative flag: 0

Test Result:

```
//NOR: 4294967041 nor 241 = 14
#10 i_datain<=32'b000000_00011_00010_00001_00000_100111;
gr1<=32'b1111_1111_1111_1111_1111_1111_0000_0001;
gr2<=32'b0000_0000_0000_0000_0000_0000_1111_0001;

//NOR: 1 nor 2**32-1 = 0
#10 i_datain<=32'b000000_00011_00010_00001_00000_100111;
gr1<=32'b0000_0000_0000_0000_0000_0000_0000_0001;
gr2<=32'b1111_1111_1111_1111_1111_1111_1111_1111;
```

[illegible]

2.4.11. OR / ORI

Hardware: OR gates

Theory: OR can be done by bitwise operation. imm should be zero-extended.

Registers: reg A, reg B, reg C

Result: $c = \text{gr1} \mid \text{gr2} / c = \text{gr1} \mid [\text{zero-extended}] \text{imm}$


Overflow flag: 0

Zero flag: Set if reg C = 0.

[illegible]

2.4.14. SLT / SLTI

Hardware: 32-bit full adder, invertor

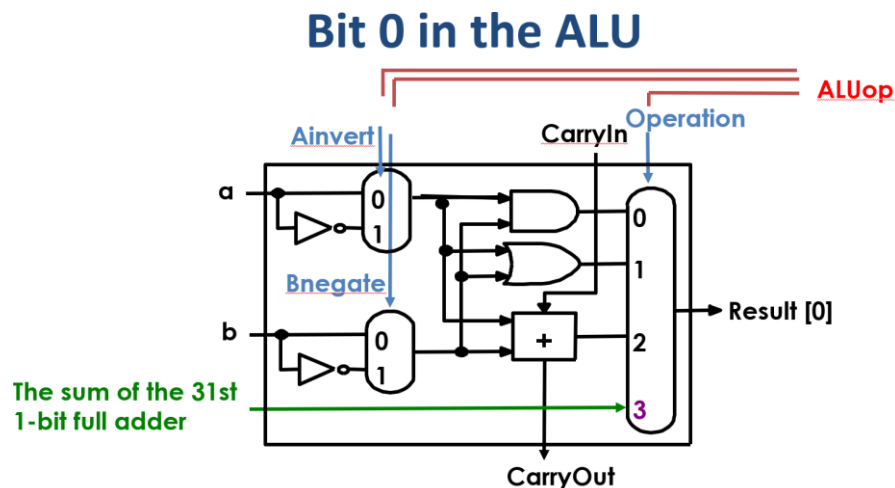

Theory:

For the ALU, SLT is based on `reg_A - reg_B`. If the first operand (`reg_A`) is less than the second operand (`reg_B`), then `reg_A - reg_B` will be negative. In other words, the sum of the 31st 1-bit full adder will be 1. Otherwise, it will be 0.

As for the result of SLT, the first 31 bits are always 0, while the 32nd bit is the same as the sum of the 31st 1-bit full adder.

Registers: reg A, reg B, reg C

Result: $c = \text{gr1} < \text{gr2} / c = \text{gr1} < [\text{sign-extended}] \text{imm}$

Overflow flag: 0

Zero flag: Set if reg C = 0.

Negative flag: 0


```
//SLTIU: 7 < 2**15 : 1
#10 i_datain<=32'b001011_00011_00010_1000000000000000;
gr1<=32'b0000_0000_0000_0000_0000_0000_0000_0111;
gr2<=32'b1111_1111_1111_1111_1111_1111_1111_1111;

//SLTU: 7 < 2**32-1 : 1
#10 i_datain<=32'b000000_00011_00010_00001_00000_101011;
gr1<=32'b0000_0000_0000_0000_0000_0000_0000_0111;
gr2<=32'b1111_1111_1111_1111_1111_1111_1111_1111;
```

[illegible]

2.4.16. LW / SW

Hardware: 32-bit full adder

Theory: For the ALU, LW and SW is the same as ADDI

Registers: reg_A, reg_B, reg_C

Result: $c = \text{gr1} + [\text{sign-extended}] \text{ imm}$

Overflow flag: Set if an overflow occurs.

Zero flag: Set if reg_C = 0.

Negative flag: reg_C[31]

Test Result:

```
//LW: 8 + 4 = 12
#10 i_datain<=32'b100011_00011_00010_0000000000000100;
gr1<=32'b0000_0000_0000_0000_0000_0000_0000_1000;
gr2<=32'b0000_0000_0000_0000_0000_0000_0000_0100;

//SW: 2147483648 + -4 = 2147483644
#10 i_datain<=32'b100011_00011_00010_1111111111111100;
gr1<=32'b1000_0000_0000_0000_0000_0000_0000_0000;
gr2<=32'b0000_0000_0000_0000_0000_0000_0000_0100;
```

[illegible]

2.4.17. SLL / SLLV

Hardware: 32-bit shift register


```
#10 i_datain<=32'b0000000_00011_00010_00001_00000_000111;  
gr1<=32'b1000_0000_0000_0000_0000_0000_0000_0000;  
gr2<=32'b0000_0000_0000_0000_0000_0000_0001_0101;
```

[illegible]

2.5.Discussion & Further Improvement

In the testbench, three pieces of data are updated each time:

i_datain, gr1, gr2

Then, they are processed in the following order:

1. The main module decodes `i_datain` into `opcode`, `funct`, and `imm`.
2. The control module generates `alusrc` and `aluctr` according to `funct` and `opcode`.
3. The main module assigns `gr2` or `imm` to register `operand2`.
4. The main module sends `aluctr`, `gr1`, and `operand2` to the ALU.

In the ALU module, I used the following statement:

always @(aluctr, gr1, operand2)

where `aluctr` is the control signal, `gr1` is general register 1, and `operand` is general register 2 or sign-extended immediate.

When testing my Verilog code, I found out that the four ALU inputs were not synchronized. In the ALU, `gr1` is updated earlier, while `aluctr` and `operand2` are updated a little bit later. Hence, for an instant, the ALU will generate the result from the current `gr1` and the previous `aluctr` and `operand2`. However, this instant is so short that the monitor will automatically ignore the result. So, this asynchronous issue will not affect the result.

In the project 4, a clock signal will be added to the ALU. Naturally, this problem will be completely fixed.